
Automotive								lantu	Niv	mber
Sect	tion II (continued)									mber
Que (a)	when disconnecting or connecting an autor				st and	d rep	olaceo	d las	t	1
									· ·	
(b)	What does CCA refer to in an automotive	battery?	•••••							1

Question 19 continues on page 14

315 - 13 -

Question 19 (continued)

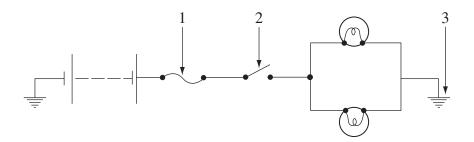(c) This diagram shows some components in an electrical circuit.



3


1

1


Complete the table naming and describing the function of each numbered component.

Component	Name	Function
1		
2		
3		

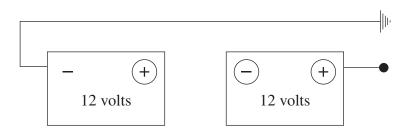(d) In the diagram below, draw lines to show how to connect the terminals to increase battery output voltage to 24 volts.



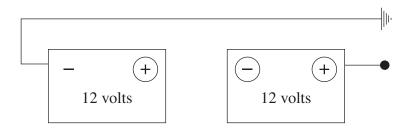(e) In the diagram below, draw lines to show how to connect the terminals to maintain battery output voltage at 12 volts.



End of Question 19