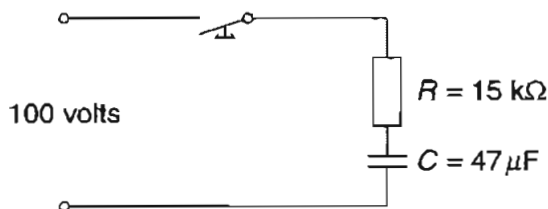


**Question 20** (5 marks)

An electrical circuit is shown.



Calculate, showing all working:

- (a) the time constant for the circuit; 2

$$\tau = RC$$

$$\tau = 15000 \times 47 \times 10^{-6}$$

$$= 0.705 \text{ seconds}$$

∴ 1 time constant = 0.705 sec

- (b) the maximum circuit current; 1

$$V = IR$$

$$I = \frac{V}{R} = \frac{100}{15000}$$

$$= 6.67 \text{ mA}$$

- (c) the value of resistance to be added to change the time constant to one second. 2

$$\tau = RC \quad (C = 47 \mu\text{s})$$

$$\frac{\tau}{C} = R$$

$$R = \frac{1}{47 \times 10^{-6}}$$

$$R = 21276.59574 \Omega$$

$$= 21.28 \text{ k}\Omega \text{ (2 dp)}$$